
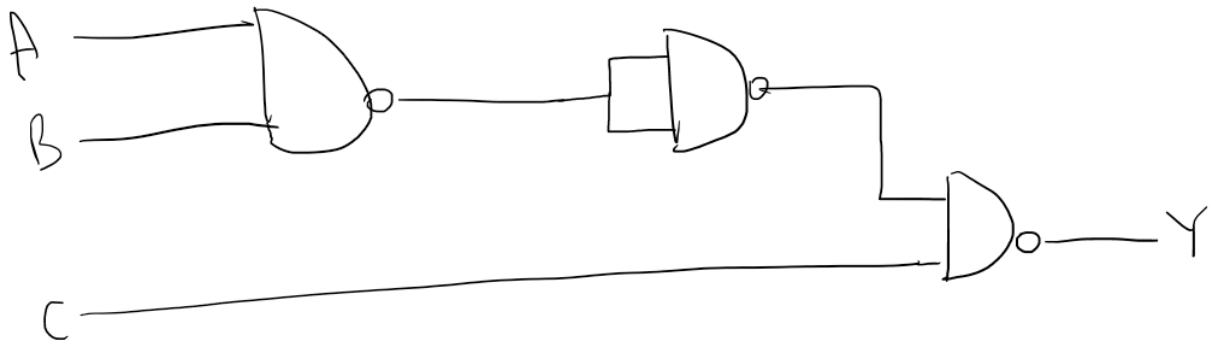


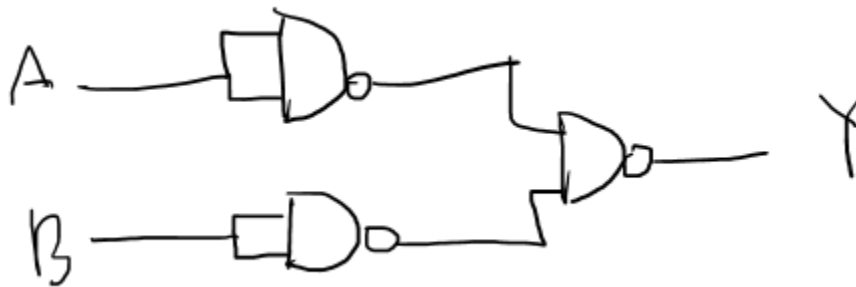1. An inverter can be implemented with 1 input connected to both the terminals. Another way can be to connect one of the inputs to power which would result in a constant 1 state and the input signal to the other.




2.




3.

4. $(A+B) \cdot \neg(AB)$

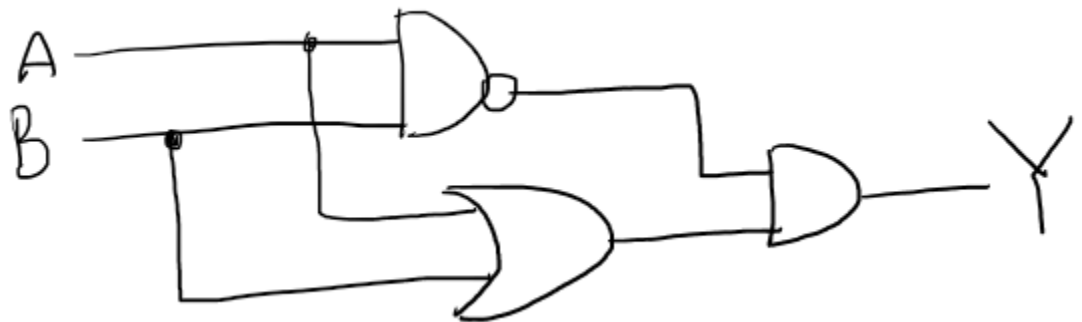

a.

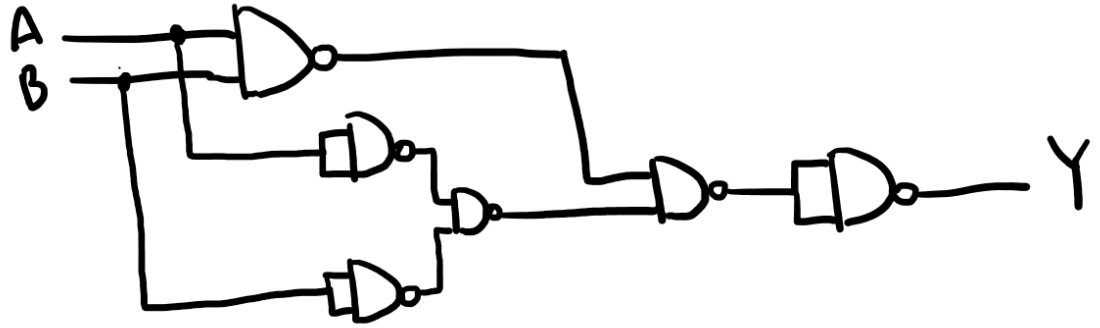


b.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

c.

The common name of this function is XOR
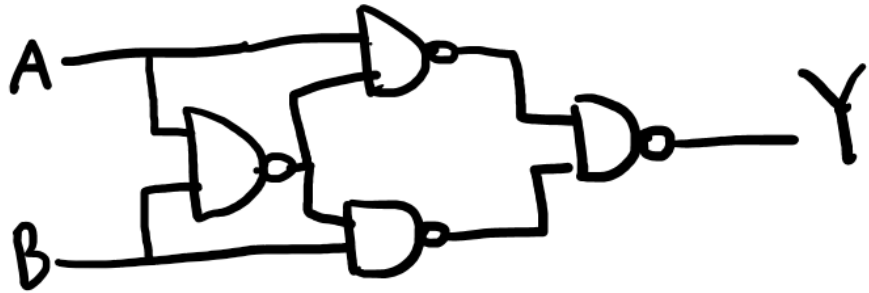
$$\begin{aligned}
 Z = f(A, B) &= (A+B) \overline{AB} \\
 &= A(\overline{AB}) + B(\overline{AB}) \\
 &= A\overline{B} + \overline{A}B
 \end{aligned}$$



d.